

## Exercise 2:

$$1) \frac{V_2 - V_1}{R_2} = I$$

$$\frac{0.1}{R_2} = 10^{-6}$$

$$R_2 = \frac{0.1}{10^{-6}} = 100 \text{ k}\Omega$$

$$2) \frac{R_4}{R_3 + R_4} = \frac{1}{10}$$

$$\frac{R_4}{R_3} = \frac{1}{9}$$

we can choose

$$R_4 = 22 \text{ k}\Omega, R_3 = 200 \text{ k}\Omega$$

which yields:

$$\frac{22}{22+200} \cdot 5 = 0.4955 \text{ V}$$

$$3) Q = CV$$

$$I = C \dot{V}$$

$$I = SCV$$

$$Z_C = \frac{1}{SC}$$

$$\left| \frac{R}{R + \frac{1}{j\omega C}} \right| = \frac{1}{2}$$

$$\left| \frac{j\omega RC}{j\omega RC + 1} \right| = \frac{1}{\sqrt{2}}$$

$$\frac{(j\omega RC)^2}{1 + (j\omega RC)^2} = \frac{1}{2}$$

$$2(j\omega RC)^2 = 1 + (j\omega RC)^2$$

$$j\omega RC = 1$$

$$RC = \frac{1}{\omega}$$

$$= \frac{1}{2\pi \cdot 100}$$


$$= 1.59155 \text{ E-3 s}$$

$$R_5 = 1.6 \text{ k}\Omega$$



$$C_1 = 1 \text{ nF are close}$$

$R_5 = 1.6 \text{ k}\Omega$   
 $C_1 = 1 \text{ nF}$  are close


4)

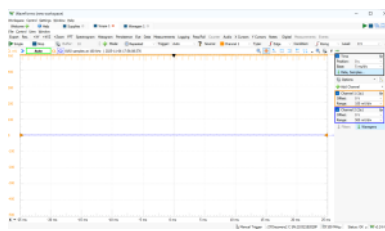

5)

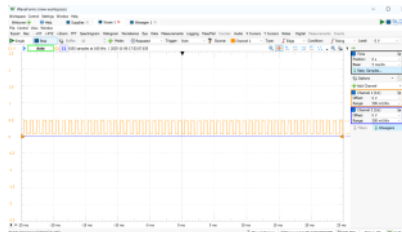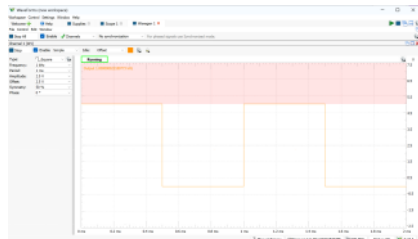

6)

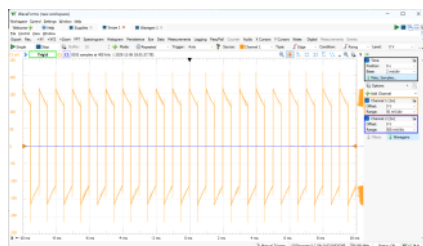

7)



Exercise 3:

$$1) \frac{R_8}{R_8 + R_7} = \frac{1}{2}$$

$$R_8 = R_7$$

$$R_8 = R_7 = 10 \text{ k}\Omega \text{ works}$$

The circuit becomes:

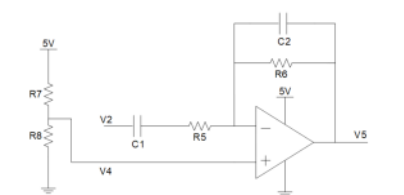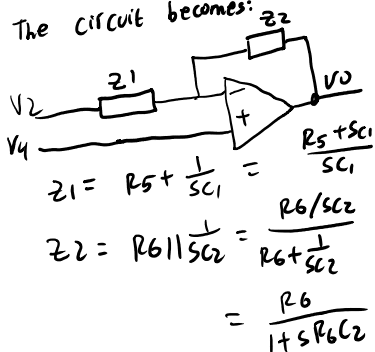

$$V_0 = V_4 \left( 1 + \frac{Z_2}{Z_1} \right) - V_2 \left( \frac{Z_2}{Z_1} \right)$$

so

$$V_0 = V_4 \left(1 + \frac{z_2}{z_1}\right) - V_2 \left(\frac{z_2}{z_1}\right)$$

$$V_0 = V_4 + \frac{z_2}{z_1} (V_4 - V_2)$$

we want  $\left|\frac{z_2}{z_1}\right| = 10$

$$\frac{\frac{R_6}{1 + sR_6C_2}}{R_5 + \frac{1}{sC_1}} = \frac{R_6 \left(\frac{1}{1 + sR_6C_2}\right)}{R_5 \left(1 + \frac{1}{sR_5C_1}\right)}$$

$$= \frac{R_6}{R_5} \left(\frac{sR_5C_1}{1 + sR_5C_1}\right) \left(\frac{1}{1 + sR_6C_2}\right)$$

so we pick  $\frac{R_6}{R_5} = 10$

$$R_6 = 16 \text{ k}\Omega, R_5 = 1.6 \text{ k}\Omega$$

2)  $\left|\frac{1}{1 + sR_6C_2}\right| = \frac{1}{\sqrt{2}}$

$$2 = 1 + (\omega R_6 C_2)^2$$

$$1 = \omega R_6 C_2$$

$$C_2 = \frac{1}{R_6 \omega}$$

$$= \frac{1}{16 \text{ E}3 \cdot 16 \text{ E}3 \cdot 2\pi}$$

$$= 0.622 \text{ nF}, \text{ since } \omega > 16 \text{ E}3:$$

pick




$$C_2 \leq 0.622 \text{ nF} = 620 \text{ pF}$$

Let's choose the highest capacitor we have, which is

$C_2 = 100 \text{ pF}$ , this has a cut off frequency of:

$$\omega = \frac{1}{RC} = \frac{1}{16 \text{ E}3 \cdot 100 \text{ E}12} = 625 \text{ E}3 \text{ rad/s} = 99.5 \text{ kHz}$$

3)

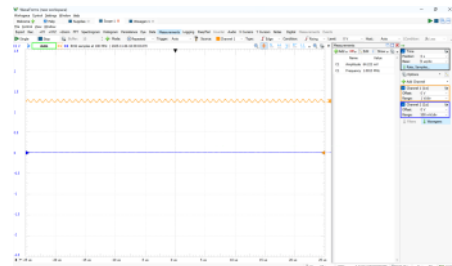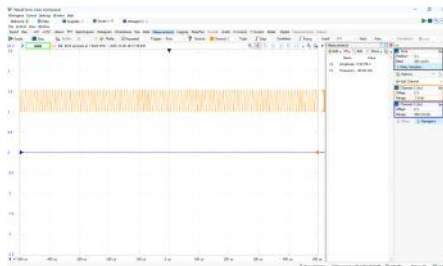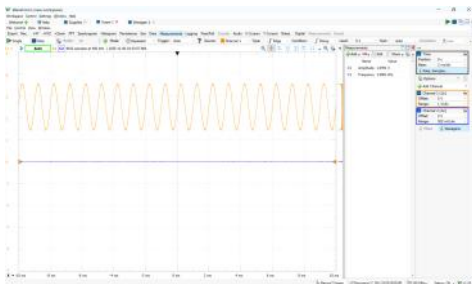

4)

5)

6)

Phase 2:

Exercise 4:

$$1) V_6 = \frac{R_9}{R_9 + \frac{1}{C_5}} V_5$$

$$R_9 = 1.6 \text{ k}\Omega, C_1 = 14 \text{ F}$$

$$2) V_7 = V_6 \left( 1 + \frac{R_{11}}{R_{10}} \right)$$

$$\frac{R_{11}}{R_{10}} = 10$$

$$R_{10} = 1 \text{ k}\Omega, R_{11} = 10 \text{ k}\Omega \text{ works}$$

$$3) V_8 = \frac{\frac{1}{sC_4}}{\frac{1}{sC_4} + R_{12}} V_7$$

$$V_8 = \frac{1}{1 + R_{12} sC_4} V_7$$

$$\left| \frac{1}{1 + R_{12} sC_4} \right| = \frac{1}{\sqrt{2}}$$

$$1 = R_{12} C_4 \omega$$

$$R_{12} C_4 = \frac{1}{\omega}$$

$$= \frac{1}{1.6 \cdot 2\pi}$$

$$= 9.95 \text{ E-}2$$

$$C_4 = 100 \text{ nF}$$

$$R_{12} = 1 \text{ M}\Omega$$

4)

